

DEVELOPMENT AND INTEGRATION
OF A LOW COST, HIGH VOLTAGE
POWER SUPPLY INTO A THIN FILM
DEPOSITION SYSTEM



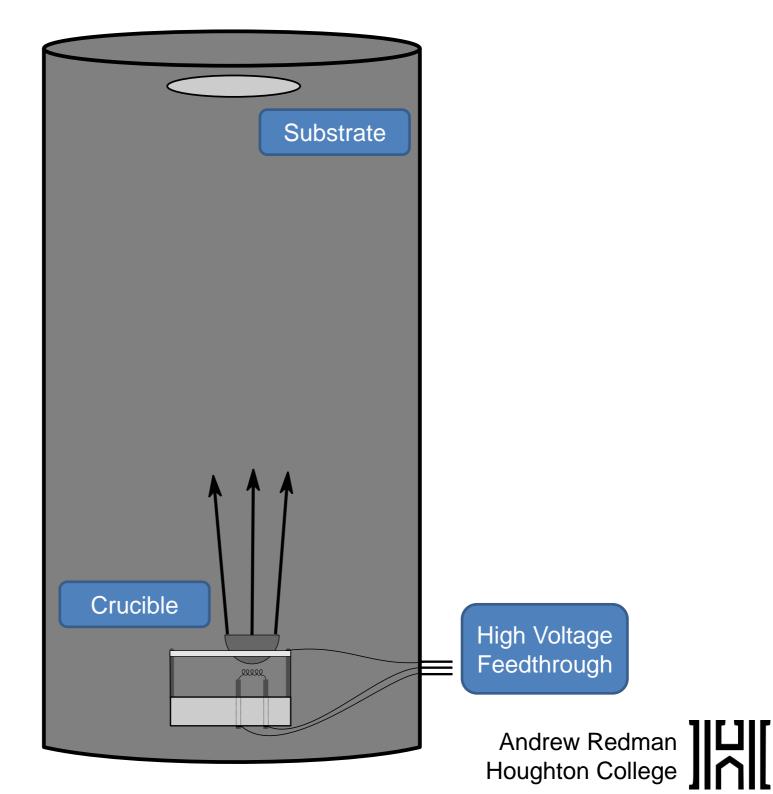
## Thin Film Applications

- Transistors
- Semiconductors
- Microcontrollers
- Computer Chips











#### The Crucible

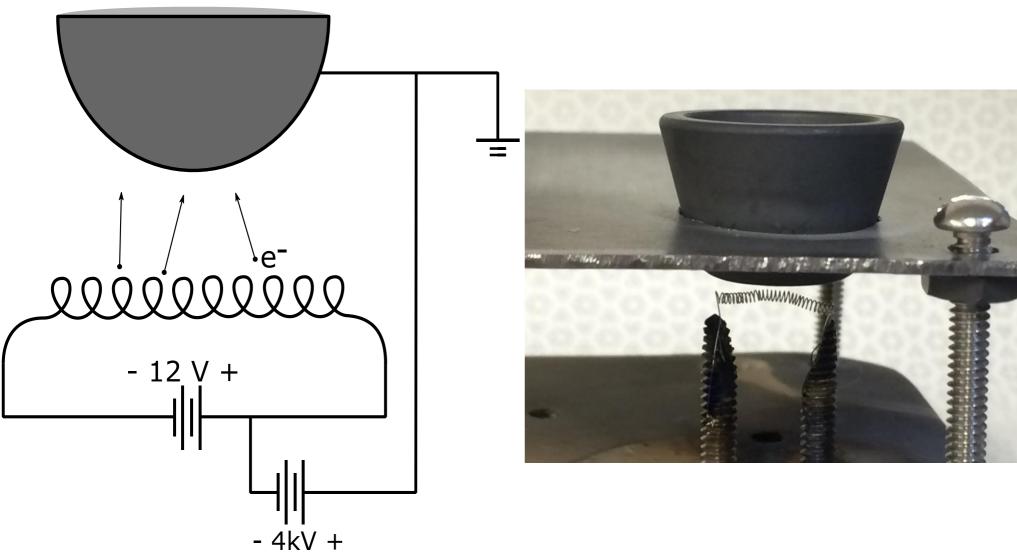

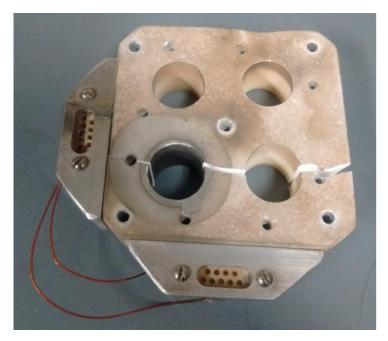










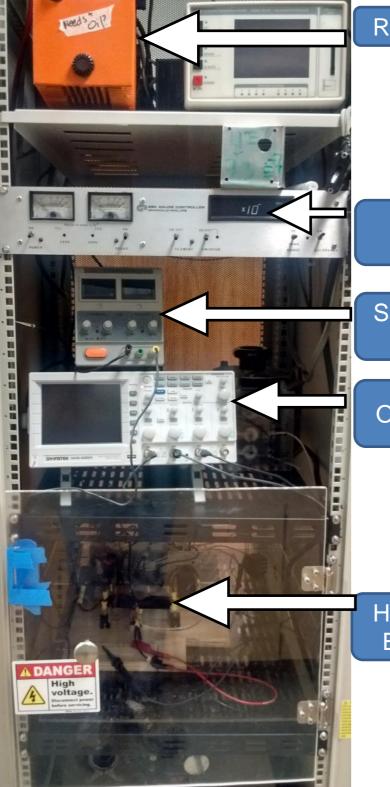

Rough Pump

Turbo Pump


Pressure Gauge

Safety Power Supply

Oscilloscope

High Voltage Feedthrough


High Voltage Electronics

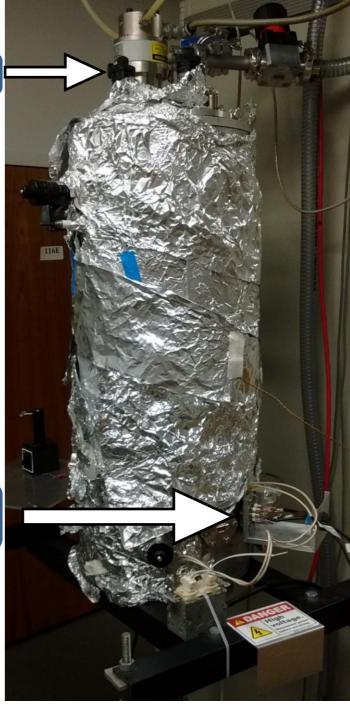


Andrew Redman Houghton College




# Original Circuit Design

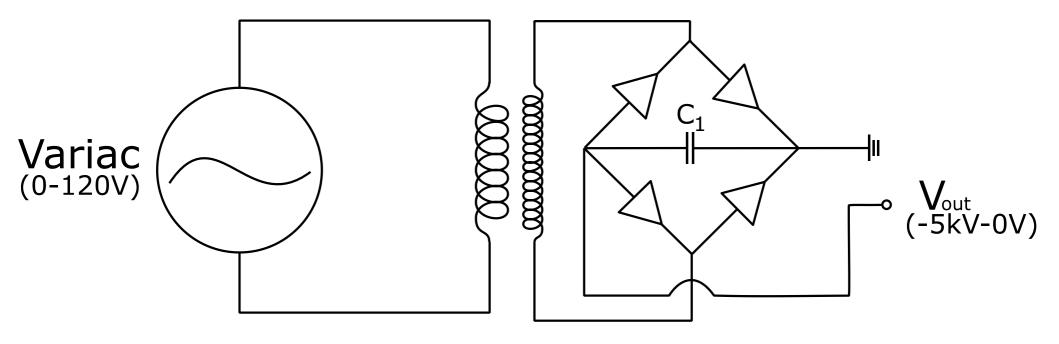



# Original Circuit Design

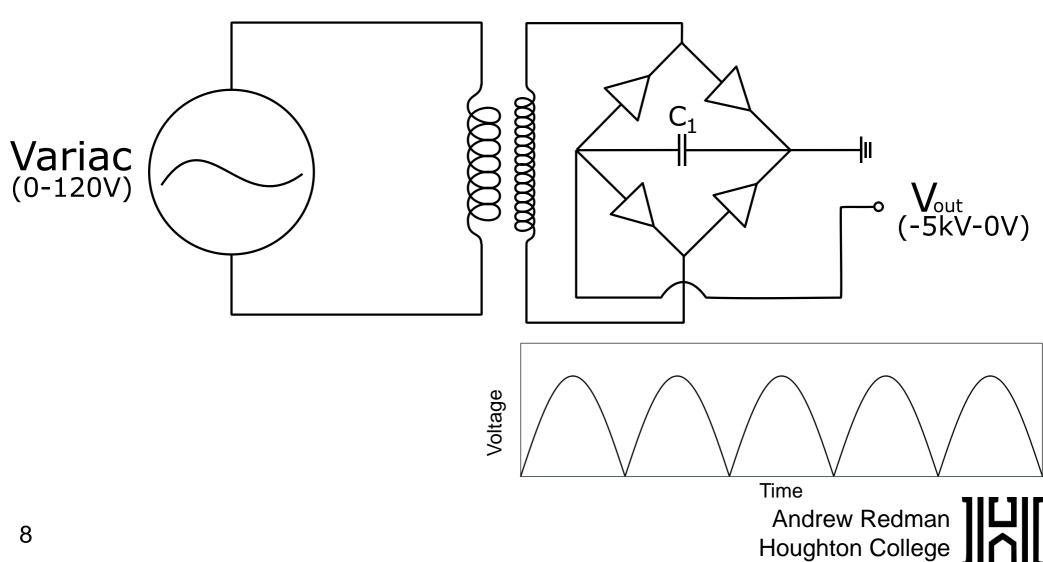


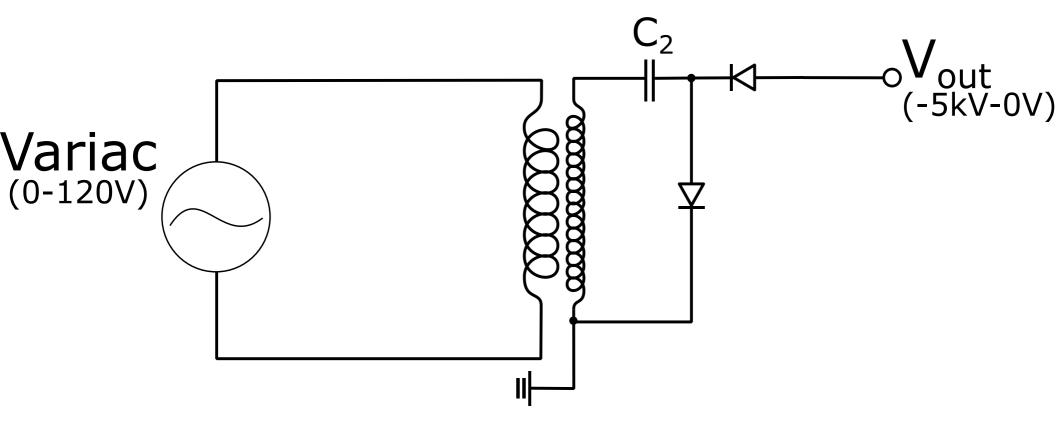





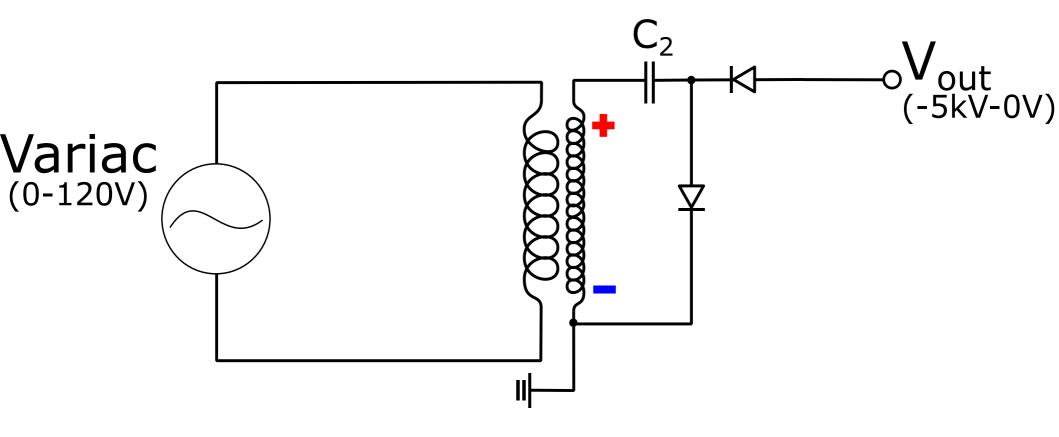


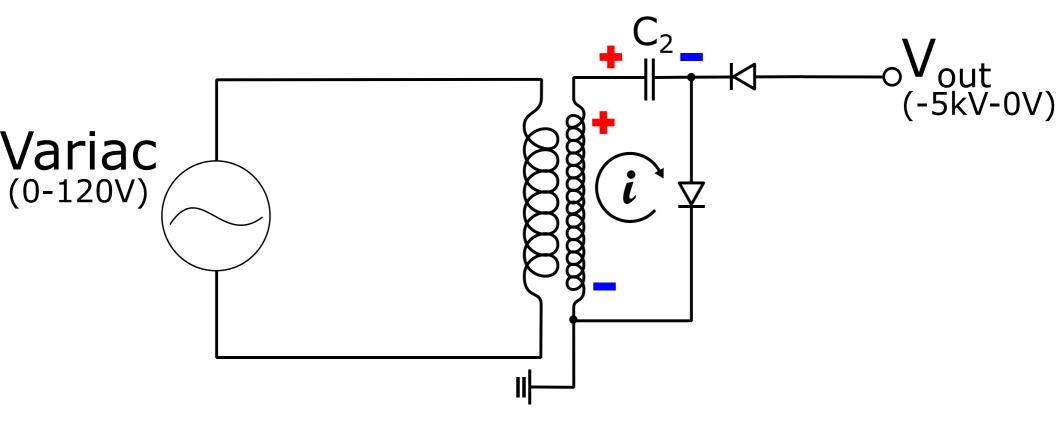

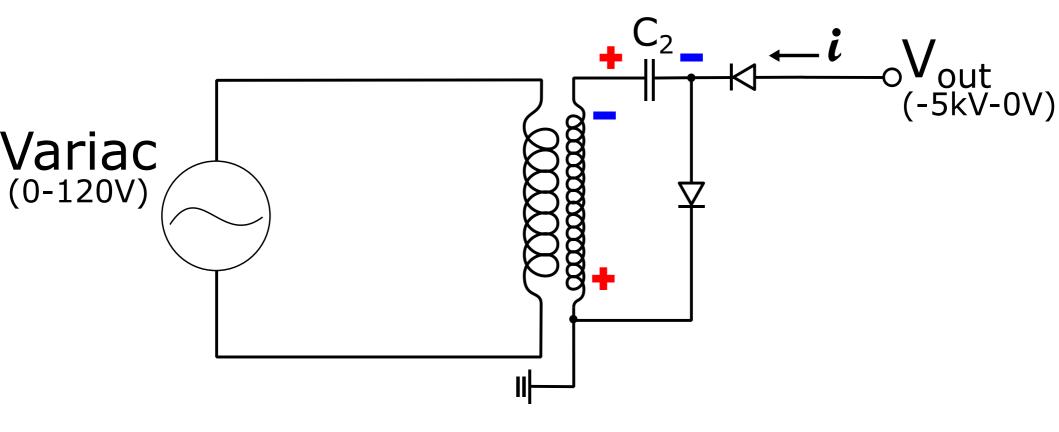


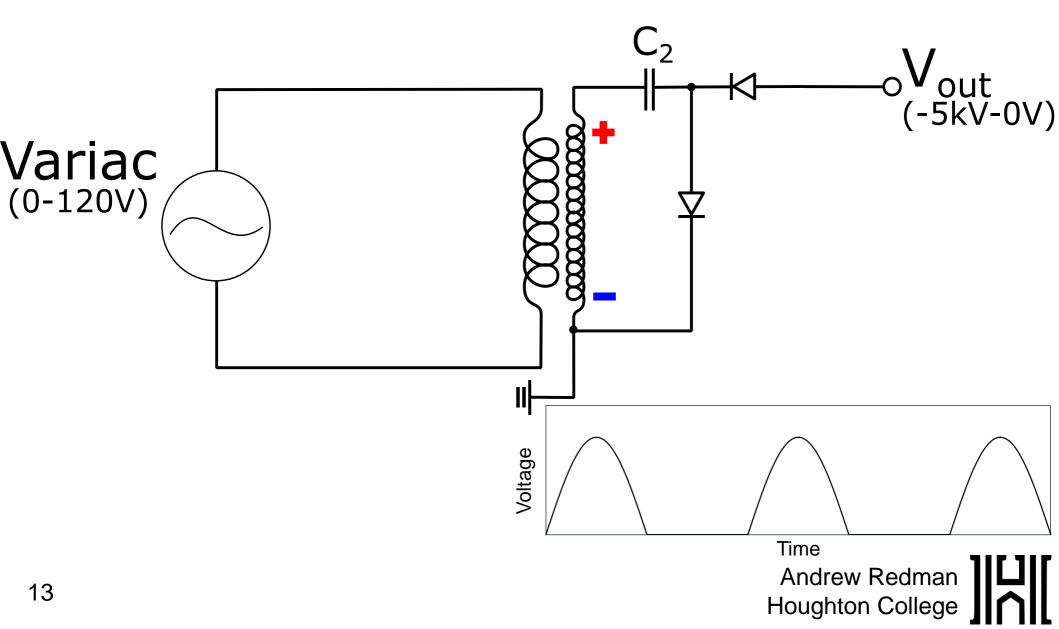

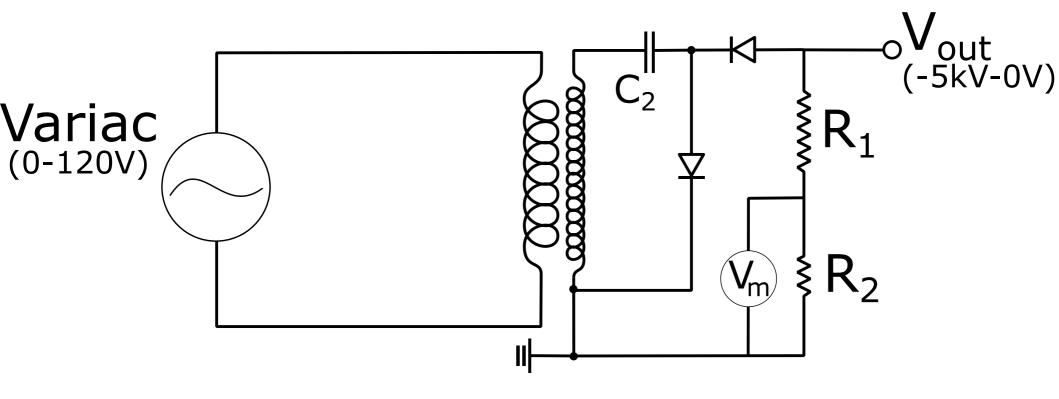


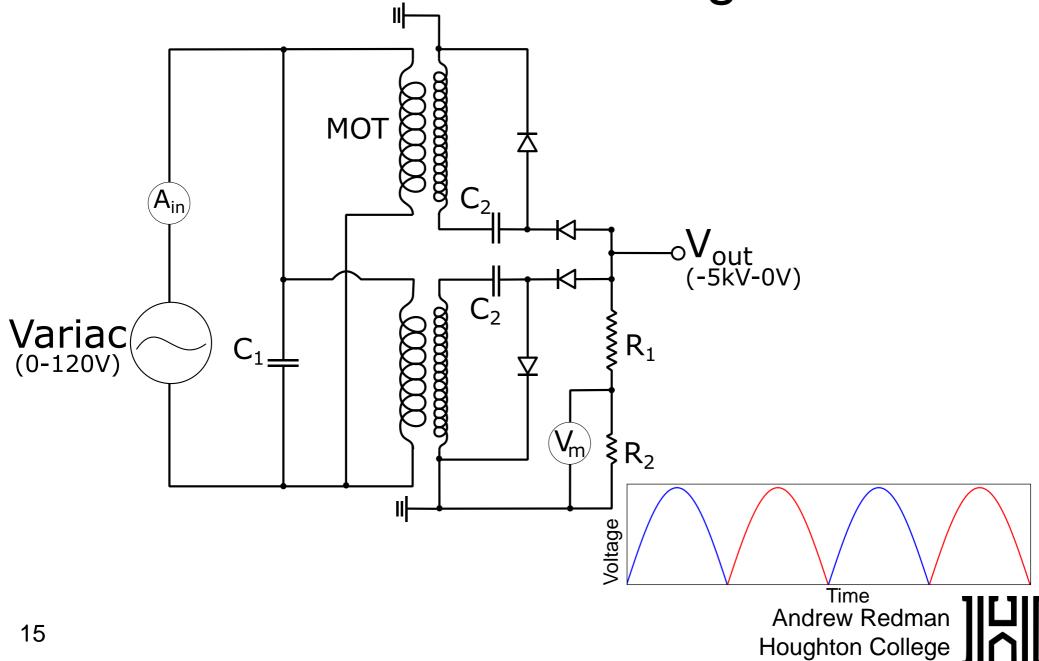


#### Phase Difference

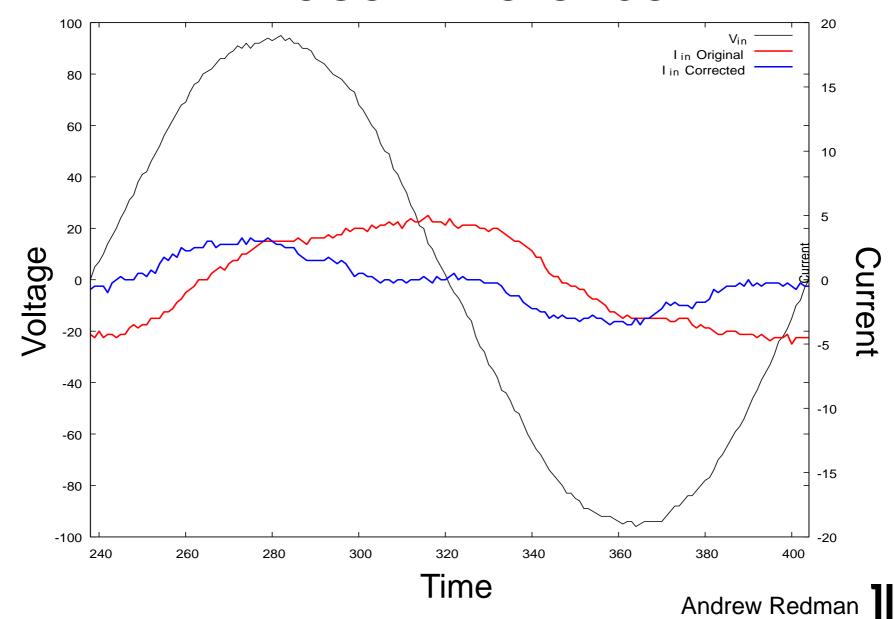


Houghton College

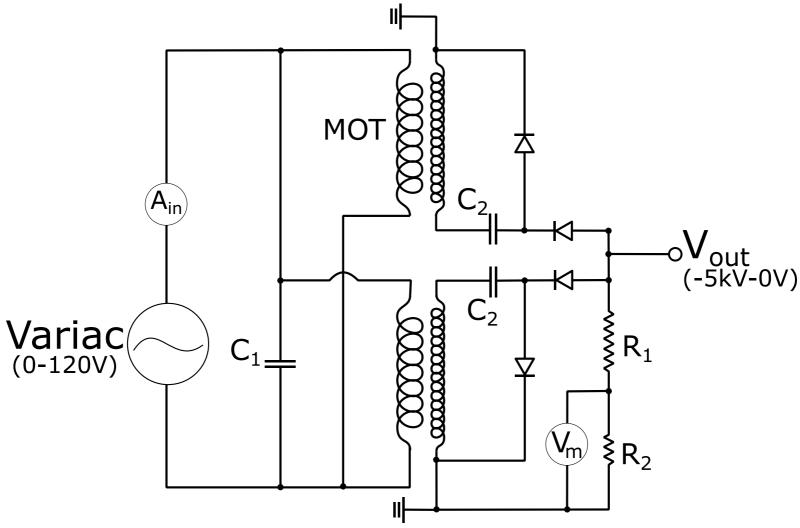

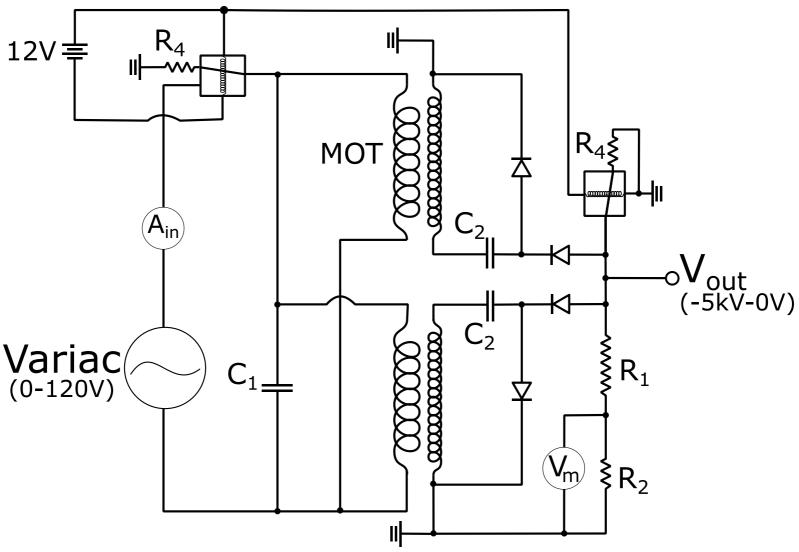



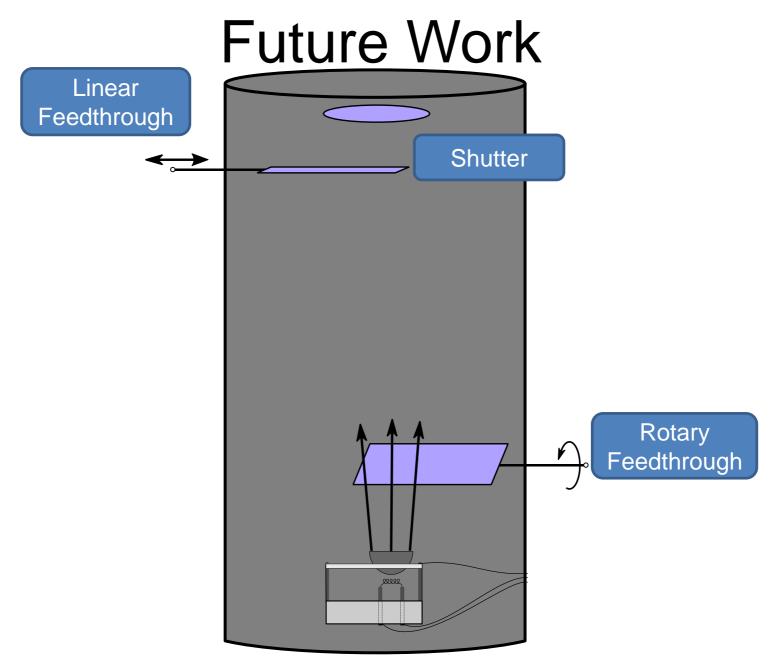



# Questions



#### Phase Correction

$$\frac{1}{Z_{T}} = \frac{1}{Z_{L}} + \frac{1}{Z_{C}}$$

$$z_{L} = \frac{V}{I}(\cos(\phi) - i\sin\phi)$$
  $Z_{c} = i\omega C$ 

$$\frac{I}{V \cdot 2\pi f} \sin \phi = C = 49 \,\mu F$$